

Roll No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

SHAMBHUNATH INSTITUTE OF ENGINEERING AND TECHNOLOGY, PRAYAGRAJ

Subject Code: **BEE-101**Subject: **Fundamentals of Electrical Engineering**Course: **B.Tech.**

SEMESTER: I

FIRST SESSIONAL EXAMINATION, ODD SEMESTER, (2024-2025)

Time –1hr 30 min




Branch: CS

Maximum Marks – 30

NOTE: (Attempt all questions)**1. Attempt any FIVE questions.**

Q. N.	QUESTION	Marks	CO	BL
a.	Explain the followings. (i) Active element (ii) Passive element	2	CO1	BL2
b.	State and explain Kirchhoff's voltage law.	2	CO1	BL2
c.	Distinguish between mesh and loop of network.	2	CO1	BL4
d.	Distinguish between node and junction of network.	2	CO1	BL4
e.	Explain the followings. (i) Unilateral element (ii) Bilateral element	2	CO1	BL2
f.	Explain the followings. (i) Ideal voltage source (ii) Ideal current source	2	CO1	BL2

2. Attempt any ONE of the following.

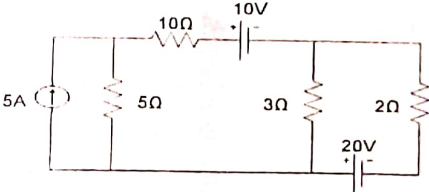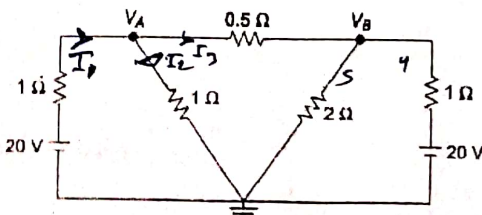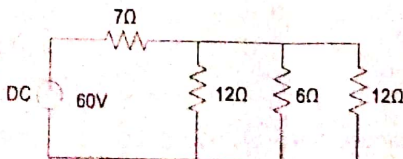Q. N.	QUESTION	Marks	CO	BL
a.	Using mesh current method, find the current in, and voltage across the 2Ω resistance in the following figure. 	5	CO1	BL3
b.	Determine the current by Nodal method, through 2Ω resistor for the network shown below. 	5	CO1	BL3
c.	In the network, find the power delivered by the source using the nodal analysis. 	5	CO1	BL3

P.T.O

3. Attempt any FIVE questions.

Q. N.	QUESTION	Marks	CO	BL
a.	What is the real power consumed by a pure capacitor?	2	CO2	BL1
b.	Define form factor and peak factor.	2	CO2	BL1
c.	What do you mean by alternation of sinusoidal quantity?	2	CO2	BL1
d.	Define average value of sinusoidal wave.	2	CO2	BL1
e.	Write the equation of voltage and current for pure inductive circuit.	2	CO2	BL1
f.	Draw and define impedance triangle of R-L series circuit.	2	CO2	BL1

4. Attempt any ONE of the following.

Q N	QUESTION	Marks	CO	BL
a.	Determine the mathematical relationship between phase and line quantities in a 3-phase star configuration with the help of phasor diagram.	5	CO2	BL5
b.	Determine the mathematical expression for instantaneous power and average power in the case of R and L elements connected in series across a single phase Ac supply of voltage $v = V_m \sin \omega t$.	5	CO2	BL5
c.	A coil of resistance 40Ω and inductance 0.75 H forms part of a series circuit for which resonant frequency is 55 Hz . If the supply is 250 V , 50 Hz , find- (i) Line current (ii) Power factor (iii) Power consumed	5	CO2	BL3

Bloom's Taxonomy Level (BL) :-

Remember (L1), Understanding (L2), Apply (L3), Analyze (L4), Evaluating (L5), Creating (L6)
