

**SHAMBHUNATH INSTITUTE OF ENGINEERING AND TECHNOLOGY**

**Subject Code: BEC-201**

**Subject: Fundamentals of Electronics Engineering**

**Course: B.Tech.**

**Semester: 2<sup>nd</sup>**

**FIRST SESSIONAL EXAMINATION, EVEN SEMESTER, (2024-2025)**

**Branch: (CS, CE, EC, ME, EE)**

**Time -1 hr.**

**Maximum Marks – 15**


**1. Attempt ALL questions:**

Q N	QUESTIONS	Marks	CO	BL
a.	Sketch the circuit of summing op-amp in inverting and non-inverting form.	1	CO3	L2
b.	An operational amplifier has differential gain of 200 and CMRR of 90 dB, input voltage are 200 $\mu$ V and 110 $\mu$ V. Determine the output voltage.	1	CO3	L3
c.	Define CMRR and slew rate of operational amplifier.	1	CO3	L1
d.	Explain unity gain amplifier.	1	CO3	L1
e.	Write the ideal characteristics of Op-Amp.	1	CO3	L2

2. Attempt any ONE of the following:

Q N	QUESTIONS	Marks	CO	BL
a.	<p>Derive the expression for gain of Op-Amp as non-inverting amplifier. Determine the output voltage (<math>V_o</math>) of the given circuit.</p>	5	CO3	L3
b.	<p>Explain the concept of virtual ground in Op-Amp. Determine the output voltage (<math>V_o</math>) for given circuit.</p>	5	CO3	L3

3. Attempt any ONE of the following:

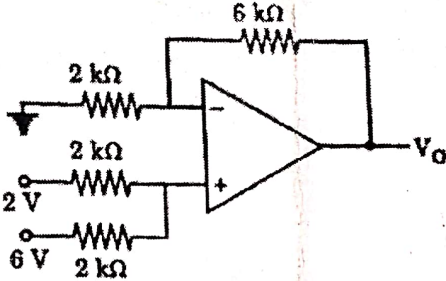Q N	QUESTIONS	Marks	CO	BL
a.	<p>Explain any two with the help of necessary diagram:</p> <p>I. Integrator and Differentiator circuit of Op-Amp.</p> <p>II. Differential amplifier in two modes of operation.</p> <p>III. Inverting and non-inverting comparator circuit of Op-Amp.</p>	5	CO3	L1
b.	<p>Define Op-Amp with the help of block diagram. Determine the output voltage (<math>V_o</math>) for given circuit.</p> 	5	CO3	L1

**Bloom's Taxonomy Level (BL):**

Remember (L1)

Understanding (L2)

Apply (L3)

Analyze (L4)

Evaluating (L5)

Creating (L6)